

TD 1

EXERC 1

① At $T = 300 \text{ K}$

$$B = 7,3 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$$

$$E_g = 1,2 \text{ eV}$$

$$K = 8,62 \times 10^{-5} \text{ eV/K}$$

$$n_i = BT^{3/2} e^{-E_g/2KT}$$

$$= 7,3 \times 10^{15} \times 300^{3/2} \times e^{-1,2/2 \times 8,62 \times 10^{-5} \times 300}$$

$$= 3,01 \times 10^9 \text{ atoms/cm}^3$$

At $T = 600 \text{ K}$

$$n_i = 7,3 \times 10^{15} \times 600^{3/2} \times e^{-1,2/2 \times 8,62 \times 10^{-5} \times 600}$$

$$= 9,84 \times 10^{14} \text{ atoms/cm}^3$$

∴ Because there is more energy to liberate the atoms from their bonds.

② pour $T = 300 \text{ K}$

$$n_n = N_d = 10^{16} \frac{\text{electrons}}{\text{atoms/cm}^3}$$

$$P_n = \frac{n_i^2}{N_d} = \frac{(3,01 \times 10^9)^2}{10^{16}}$$

$$= 906,01 \text{ holes/cm}^3$$

EXERCICE 2

① $L = 1 \mu\text{m}$, $V = 1 \text{ V}$, $M_n = 1350 \text{ cm}^2/\text{Vs}$

$$E = \frac{V}{L} = \frac{1}{1 \times 10^{-4}} = 10^4 \text{ V/cm}$$

$$\begin{aligned} V_{n\text{-drift}} &= -M_n E \\ &= -(-10^4 \times 1350) \\ &= 1,35 \times 10^7 \text{ cm/s} \end{aligned}$$

②

We want to have

$$I_n = I_p$$

$$n M_n E = p M_p E$$

$$n M_n = p M_p$$

$$\frac{n}{p} = \frac{M_p}{M_n}$$

$$\frac{n}{p} = \frac{480}{1350} = 0,356$$

$$n = 0,356 p$$

EXERCICE 3

$$T = 300 \text{ K}, N_A = 10^{18} \text{ cm}^{-3}, N_D = 10^{16} \text{ cm}^{-3}$$

$$A = 10^{-4} \text{ cm}^2$$

① $P_p = N_A = 10^{18} \text{ cm}^{-3}$

$$n_{p0} = \frac{n_i^2}{N_A} = \frac{(1,5 \times 10^{10})^2}{10^{18}}$$

$$= \underline{\underline{225 \text{ cm}^{-3}}}$$

$$n_n = N_D = 10^{16} / \text{cm}^3$$

$$p_{n0} = \frac{n_i^2}{N_D} = \frac{(1,5 \times 10^{10})^2}{10^{16}} = 2,25 \times 10^4 / \text{cm}^3$$

$$V_0 = V_T \ln \left(\frac{N_D \times N_A}{n_i^2} \right)$$

$$V_T = \frac{KT}{q} = \frac{8,62 \times 10^{-5} (\text{eV/K}) \times 300 (\text{K})}{1 \text{e}} = 0,025 \text{V} = 25 \text{mV}$$

$$V_0 = 0,025 \ln \left(\frac{10^{18} \times 10^{16}}{(1,5 \times 10^{10})^2} \right)$$

$$V_0 = 0,79 \text{V}$$

EXERCICE 4

a) $I_D = K'_n \left(\frac{W}{L} \right) V_{ov}^2$ et $K'_n = C_{ox} \mu_n$

$$V_{ov} = \sqrt{\frac{I_D \cdot 2 \cdot L}{C_{ox} \cdot \mu_n \cdot W}} = \sqrt{\frac{100 \cdot 2 \cdot 0,18}{8,6 \times 10^{-15} \times 450 \cdot 10^8 \cdot 2}} = 215,6 \text{mV}$$

$$V_{ov} = V_{ov} - V_t =$$

$$V_{GS} = V_{ov} + V_t$$

$$V_{GS} = 215,6 \times 10^{-3} + 0,5 = 0,715 \text{V}$$

$$V_{DS} = V_{ov} = 215,6 \text{mV}$$

b) $I_D = K'_n \left(\frac{W}{L} \right) \left(V_{ov} V_{DS} - \frac{1}{2} V_{DS}^2 \right)$

$$K'_n = \mu_n C_{ox} = 450 \times 10^{-4} \times \frac{8,6 \times 10^{-15}}{10^{-12}} = 450 \times 10^{-4} \times 8,6 \times 10^{-3} = 3,87 \times 10^{-4} \text{A/V}^2$$

$$\frac{W}{L} = \frac{2}{0,18} = 11,111$$

$$I_D = 50 \mu\text{A} = 50 \times 10^{-6} \text{A}$$

A/ors

$$50 \times 10^{-6} = 3,87 \times 10^{-4} \times 11,11 \left(0,215 V_{DS} - 0,5 V_{DS}^2 \right)$$

$$0,0116 = 0,215 V_{DS} - 0,5 V_{DS}^2$$

$$-0,5 V_{DS}^2 + 0,215 V_{DS} - 0,0116 = 0$$

$$V_{DS} = 0,367 \text{V}, V_{DS} = 0,0632 \text{V}$$

Donc $V_{DS} = 0,0632 \text{V}$ car $V_{DS} < V_{ov} = 0,215 \text{V}$

c) $V_{DS} = 0,3 \text{V}$, V_{GS2}

$$I_{D1} = \frac{1}{2} K'_n \left(\frac{W}{L} \right) V_{ov}^2 = \frac{1}{2} \times 3,87 \times 10^{-4} \times 11,11 \times 0,2^2$$

$$I_{D1} = 86 \mu\text{A}$$

$$\text{Pour } V_{GS2} = 0,7 + 0,01 = 0,71 \text{V}$$

$$I_{D2} = 94,8 \mu\text{A}$$

$$\Delta I_D = I_{D2} - I_{D1} = 8,8 \mu\text{A}$$

pour $V_{DS} = 0,7 - 0,01 = 0,690 \text{ V}$

$I_{D3} = 77,6 \mu\text{A}$

$\Delta I_D = I_{D3} - I_{D1}$
 $= -8,4 \mu\text{A}$

EXERCICE 5

(a)

$L_3 < L_2 < L_1$

$R = \frac{L}{K'_n W V_{OV}}$

* lorsque L augmente, la résistance aussi augment. $L \uparrow \Rightarrow R \uparrow \Rightarrow I_D \downarrow (V_G > V_{TH})$

* pour $V_{GS} < V_{TH} \Rightarrow I_D = 0$

(b) $I_D = K'_n \frac{W}{L} \left(V_{OV} V_{DS} - \frac{1}{2} V_{DS}^2 \right)$

(c)

(c) $W_3 > W_2 > W_1$

EXERCICE 6

* Assuming Saturation

$V_{DD} = 1,8 \text{ V}, \frac{W}{L} = \frac{2}{0,18} = 11,11, \mu C_{ox} = 100 \times 10^{-6} \text{ A/V}^2$

$V_{GS} = V_G - V_S = 1 - 0$

$V_{DS} = 1$ alors $V_{OV} = V_{GS} - V_{TH}$
 $= 1 - 0,4 = 0,6$

$I_D = \frac{1}{2} K'_n \frac{W}{L} V_{OV}^2$
 $= \frac{1}{2} \times 100 \times 10^{-6} \times 11,11 \times 0,6^2$

$I_D = 2 \times 10^{-4} \text{ A} = 200 \mu\text{A}$

* Vérification

$V_D = V_{DD} - I_D R_D = 1,8 - (200 \times 2 \times 10^{-4})$

$V_D = 0,8 \text{ V}$

$V_{DS} = V_D - V_S = 0,8 - 0 = 0,8 > V_{OV}$

(ii) * Si $V_{GS} \uparrow \rightarrow V_{GS} = 1 + 0,01 = 1,01 \text{ V}$

$I_D = \frac{1}{2} K'_n \frac{W}{L} [1,01 - 0,4]^2$

$I_D = 206,7 \mu\text{A}$

$V_D = V_{DD} - R_D I_D$

$= 1,8 - 5 \times 10^3 \times 206,7 \times 10^{-6}$

$V_D = 0,766 \text{ V}$

$\Delta V_D = 0,8 - 0,766 = 0,034 \text{ V}$

TD 2

EXERCICE 1

① $K'_n = C_{ox} \mu_n$ $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$

Alors

$$K'_n = \frac{\epsilon_{ox} \cdot \mu_n}{t_{ox}}$$

$$= \frac{3,48 \times 10^{-11} \times 450 \times 10^{-4}}{4 \times 10^{-9}}$$

$$K'_n = 3,88 \times 10^{-4} \text{ A/V}^2$$

② $r_{bs} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)}$

$$W = \frac{L}{K'_n r_{bs} (V_{GS} - V_t)}$$

$$W = 9,28 \times 10^{-7} \text{ m} = 0,928 \mu\text{m}$$

③ $I_D = \frac{1}{2} K'_n \frac{W}{L} V_{OV}^2$

$$V_{OV} = \sqrt{\frac{2 I_D \times L}{K'_n W}} = \sqrt{\frac{2 \times 0,3 \times 10^{-3} \times 1}{3,88 \times 10^{-4} \times 20}}$$

$$V_{OV} = 0,27 \text{ V}$$

④ V_{DS} needed is 0,27 V

EXERCICE 2

② $V_{GS} < V_{TP} \Rightarrow |V_{GS}| > |V_{TP}|$

$$V_G - V_S < V_{TP}$$

$$V_G < V_{TP} + V_S$$

$$V_G < -1 + 5$$

$$V_G < 4 \text{ V}$$

③ In triode region

$$V_{DS} > |V_{TP}|$$

$$V_D - V_G > |V_{TP}|$$

$$V_D > |V_{TP}| + V_G$$

$$V_D > V_G + 1$$

④ In saturation

$$V_{DS} \leq |V_{TP}|$$

$$V_D \leq |V_{TP}| + V_G$$

$$V_D \leq 1 + V_G$$

⑤ $\lambda = 0$

$$I_D = \frac{1}{2} K'_p \frac{W}{L} |V_{OV}|^2$$

$$|V_{OV}| = \sqrt{\frac{2 I_D}{\frac{W}{L} \cdot K'_p}} = \sqrt{\frac{2 \times 75}{10 \times 60}}$$

$$|V_{OV}| = 0,5 \text{ V}$$

(ii) $|V_{OV}| = 0,5 = V_{SG} - |V_{TP}|$

$$V_{SG} = 0,5 + |V_{TP}| = 1,5 \text{ V}$$

$$V_S - V_G = 1,5$$

$$V_G = -1,5 + V_S = 3,5 \text{ V}$$

(iii) $V_D \leq 1 + V_G$

$$V_D \leq 1 + 3,5$$

$$V_D \leq 4,5$$

$$e) r_o = \frac{1}{|\lambda| I_D}$$

$$= \frac{1}{0,02 \times 75 \times 10^{-6}}$$

$$r_o = 667 \text{ K}\Omega$$

$$f) i) I_D = \frac{1}{2} K'_P \left(\frac{W}{L} \right) V_{OV}^2 (1 + |\lambda| V_{SB})$$

$$ii) V_{SB} = V_S - V_D = 5 - 3 = 2 \text{ V}$$

$$I_D = \frac{1}{2} \times 60 \times 10^{-6} \times 10 \times 0,5^2 \times (1 + 0,02 \times 2)$$

$$I_D = 78 \mu\text{A}$$

$$ii) \text{ pour } V_D = 0 \Rightarrow V_{SB} = 5 \text{ V}$$

$$I_D = \frac{1}{2} \times 60 \times 10^{-6} \times 10 \times 0,5^2 \times (1 + 0,02 \times 5)$$

$$I_D = 82,5 \mu\text{A}$$

$$iii) r_{DS} = \frac{\Delta V_{DS}}{\Delta I_D} = \frac{3}{4,5 \mu\text{A}} = 667 \text{ K}\Omega$$

EXERCICE 3

$$① R = \frac{V_{DD} - V_D}{I_D} \quad R = \frac{V_{DD} - V_D}{I_D}$$

$$I_D = \frac{1}{2} K_n V_{OV}^2 \quad = \frac{1,8 - 0,7}{0,032}$$

$$I_D = 0,032 \text{ mA} \quad R = 34,4 \text{ K}\Omega$$

② At the edge of saturation

$$V_{DS} = V_{OV} = V_{GS} - V_t \quad V_{DS} = V_D - V_S = 0$$



$$V_D = V_{GS} - V_t = 0,7 - 0,5 = 0,2 \text{ V} = V_{OV}$$

$$R_1 = \frac{V_{DD} - V_D}{I_D}$$

$$R_2 = \frac{1,8 - 0,2}{0,032 \times 10^{-3}}$$

EXERCICE 4

①

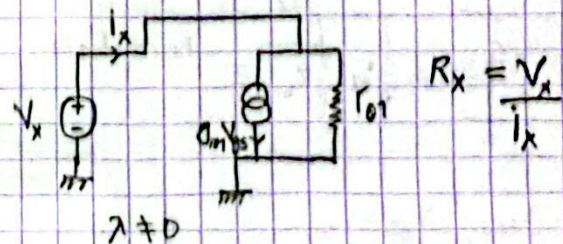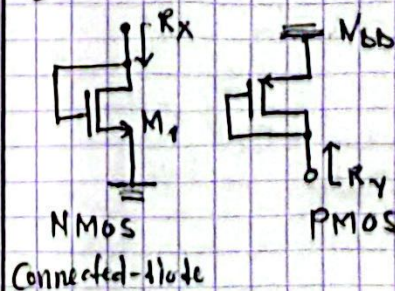


$$I_x = g_m V_{GS} + \frac{V_x}{r_{o1}} = g_m V_x + \frac{V_x}{r_{o1}}$$

$$= \left(g_m + \frac{1}{r_{o1}} \right) V_x$$


$$R_x = \frac{1}{g_m} \parallel r_{o1}$$

$$R_1 \parallel R_2$$
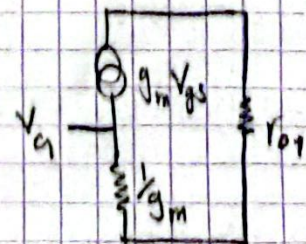
$$\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$


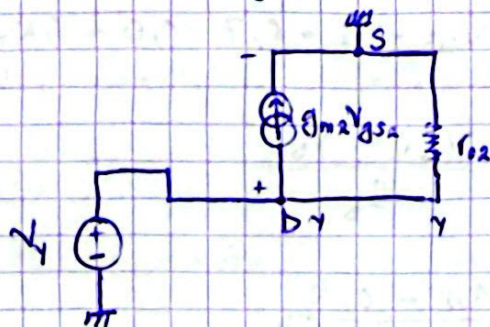
$$\left[r_{o1} \parallel \frac{1}{g_{m1}} \right] = \frac{r_{o1} \cdot \frac{1}{g_{m1}}}{r_{o1} + \frac{1}{g_{m1}}}$$




$$R_Y = \frac{V_Y}{I_Y}, \quad V_Y = r_{o2}(I_Y - g_{m2}V_{gs2})$$

$$\text{with } V_{gs2} = V_Y$$

$$V_Y(1 + g_{m2}r_{o2}) = r_{o2}I_Y$$

$$R_Y = \frac{V_Y}{I_Y} = \frac{r_{o2}}{1 + g_{m2}r_{o2}} = r_{o2} \parallel \frac{1}{g_{m2}}$$

EXERCISE 5

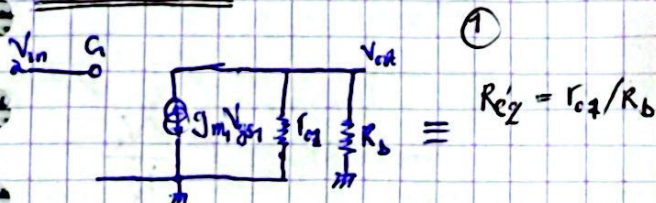

$$A_v = \frac{V_{out}}{V_{in}}; \quad V_{gs1} = V_{in}$$

$$V_{out} = -R_{eq} \cdot g_{m1}V_{gs1} = -R_{eq} \cdot g_{m1}V_{in}$$

$$A_v = -R_{eq} \cdot g_{m1}$$

$$\text{if } \lambda = 0; \Rightarrow R_{eq} = R_b \cdot \frac{1}{300 \Omega}$$

$$A_v = -g_{m1} \cdot R_b$$

$$g_{m1} = \sqrt{2 \cdot K_n I_D} = \sqrt{2 K_n \frac{W}{L} I_D} = 3,33 \cdot 10^{-3} \text{ S}^{-1}$$

$$A_v = -3,33 \cdot 10^{-3} \cdot 10^3 = -3,33 \text{ V/V}$$

②

$$V_{ds} = V_{dd} - R_b I_D$$

$$= 0,8 \text{ V}$$

$$V_{gs} = ?$$

$$I_D = \frac{1}{2} K_n' \frac{W}{L} (V_{ds} - V_t)^2$$

$$= V_{ds} = V_t + \sqrt{\frac{2 I_D}{K_n' \frac{W}{L}}} = 1,1 \text{ V}$$

$$\Rightarrow V_{ov} = V_{ds} - V_t = 0,6 \text{ V}$$

$\Rightarrow V_{ds} > V_{ds} - V_t \Rightarrow M_1$ operates in saturation region.

EXERCISE 6

①

$$V_{ov|B} = \frac{\sqrt{2 K_n R_b V_{bb} + 1} - 1}{K_n R_b}$$

$$V_{ov|B} = 0,213 \text{ V}$$

$$V_{as|B} = V_t + V_{ov|B}$$

$$= 0,4 + 0,213$$

$$V_{as|B} = 0,613 \text{ V}$$

$$* V_{bs|B} = V_{ov|B} = 0,213 \text{ V}$$

② $V_{bs|C}?$

$$I_D = K_n \left[(V_{as|C} - V_t) V_{bs|C} - \frac{V_{bs|C}^2}{2} \right]$$

$$I_D = K_n (V_{as|C} - V_t) V_{bs|C}$$

$$I_D = 4(1,8 - 0,4) V_{bs|C} = 5,6 V_{bs|C} \text{ (mA)}$$


$$* I_D = \frac{V_{bb} - V_{bs|C}}{R_b} \approx \frac{V_{bb}}{R_b} = \frac{1,8}{17,5 \cdot 10^3} = 0,1 \text{ mA}$$

$$\therefore V_{bs|C} = \frac{I_D}{5,6} = \frac{0,1 \cdot 10^{-3}}{5,6} = 18 \text{ mV}$$


EXERCICE 1

Td3

①

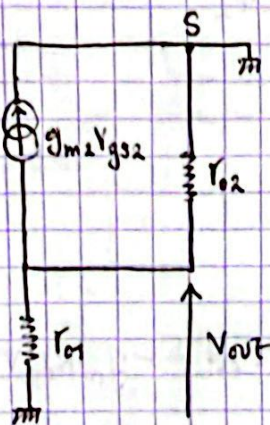
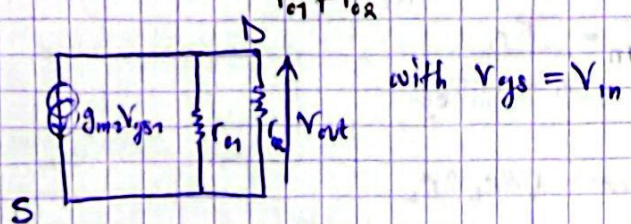
$$R_{out} = r_{o1} // r_{o2} = \frac{r_{o1} \cdot r_{o2}}{r_{o1} + r_{o2}}$$




with $V_{gs} = V_{in}$

②


$$A_v = -g_m (r_{o1} // r_{o2})$$

③

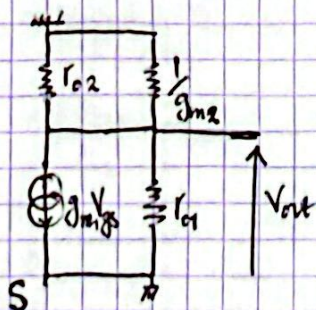

$$R_{out} = r_{o1} // \left(\frac{1}{g_{m2}} // r_{o2} \right)$$

Gain

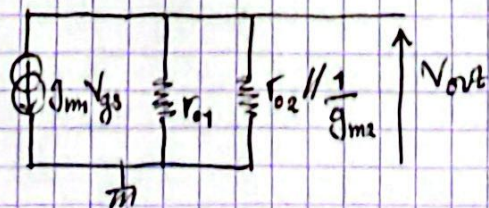

$$A_v = \frac{V_{out}}{V_{in}}$$

$$V_{in} = V_{gs}$$


$$V_{out} = -g_{m2} V_{gs} R_{out}$$

$$= -\frac{g_{m2} V_{gs} R_{out}}{V_{gs}}$$


$$A_v = -g_{m2} R_{out} = -g_{m2} (r_{o1} // (\frac{1}{g_{m2}} // r_{o2}))$$

EXERCICE 2

① $\lambda = 0$; C_{in} ?

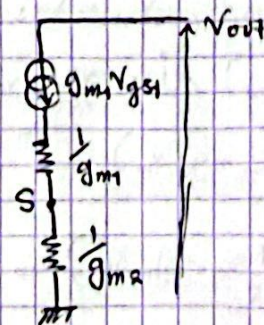
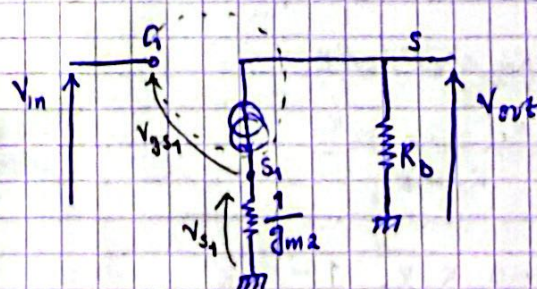
$$R_{out} = \frac{1}{g_{m1}} + \frac{1}{g_{m2}}$$



$$A_v = \frac{V_{out}}{V_{in}}$$

$$V_{in} = V_{gs1} + \frac{1}{g_{m2}} \cdot g_{m1} V_{gs1}$$

$$V_{gs1} = \frac{1}{1 + \frac{g_{m1}}{g_{m2}}} \cdot V_{in}$$

$$V_{out} = -R_D \cdot g_{m1} V_{gs1}$$

$$= -R_D \cdot g_{m1} \cdot \frac{1}{1 + \frac{g_{m1}}{g_{m2}}} \cdot V_{in}$$

$$A_v = \frac{-g_{m1} R_D}{1 + \frac{g_{m1}}{g_{m2}}}$$


$$= -\frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

CS degenerates

$$A_v = \frac{-R_D}{\frac{1}{g_{m1}} + R_S}$$

TD2: EXERCICE 7

① A_v (small-signal)

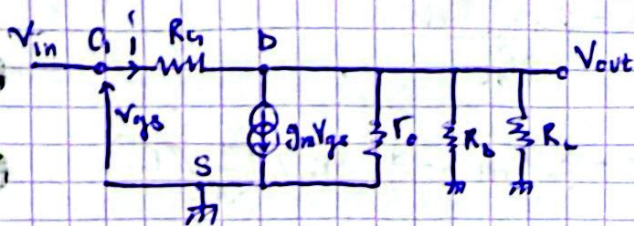

* $V_{out} = ?$

with $R_{eq} = R_L // R_b // R_o$

$$\begin{aligned} V_{out} &= R_{eq}(i - g_m V_{gs}), \quad V_{in} = V_{gs} \\ &= R_{eq}(i - g_m V_{in}), \quad i = \frac{V_{in} - V_{out}}{R_a} \\ &= R_{eq} \left(\frac{V_{in} - V_{out}}{R_a} - g_m V_{in} \right) \end{aligned}$$

$$V_{out} \left(1 + \frac{R_{eq}}{R_a} \right) = \left(\frac{R_{eq}}{R_a} - g_m R_{eq} \right) V_{in}$$

$$\frac{V_{out}}{V_{in}} = A_v = \frac{\frac{R_{eq}}{R_a} - g_m R_{eq}}{1 + \frac{R_{eq}}{R_a}}$$

with $R_{eq} = R_o // R_b // R_L$

$$A_v = \frac{R_{eq} - g_m R_{eq} R_a}{R_a + R_{eq}}$$

$$= -g_m R_L R_b \cdot \frac{1 - \frac{1}{g_m R_a}}{1 + \frac{R_L R_b}{R_a}}$$

si $g_m R_a \gg 1$

$$A_v \approx -g_m R_L R_b$$

$$A_v = \frac{R_{eq} - g_m R_{eq} R_a}{R_a + R_{eq}}$$

$$= R_{eq} \frac{1 - g_m R_{eq}}{R_a + R_{eq}}$$

$$= -g_m R_{eq} \frac{\frac{-1}{g_m} + R_{eq}}{R_a + R_{eq}}$$

* si $g_m R_b \gg 1$

$$A = -g_m R_{eq}$$

$$R'_{in} = \frac{V_{in}}{i}$$

$$i = \frac{V_{in} - V_{out}}{R_a}, \quad V_{out} = -g_m R_{eq} V_{in}$$


$$i = \frac{V_{in} (1 + g_m R_{eq})}{R_a}$$

$$R'_{in} = \frac{R_a}{1 + g_m R_{eq}}$$

$$R_{out} = R_o // R_b // R_L$$

EX 2

$$\lambda \neq 0$$

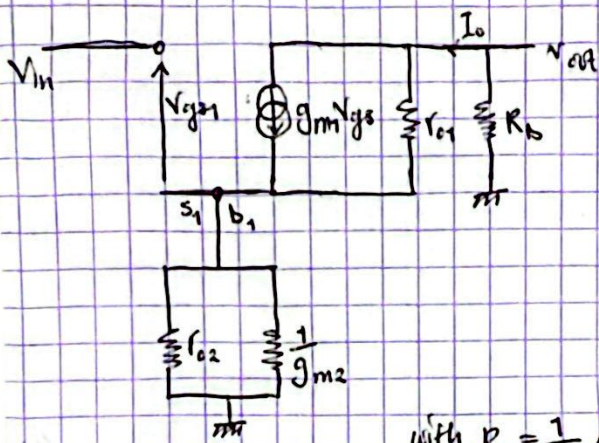

$$\text{with } R_s = \frac{1}{g_{m2}} \parallel r_{o2}$$

Gain A_v ?

$$V_{out} = -R_b I_o, \quad I_{R_s} = I_o = -\frac{V_{out}}{R_b}$$

* Calculate I_{o1}

$$I_{o1} = I_o - g_{m1} V_{gs1}$$

with

$$V_{gs1} = V_{in} - V_{s1}, \quad V_{s1} = R_s I_o \\ = -\frac{R_s}{R_b} V_{out}$$

$$I_{o1} = -\frac{V_{out}}{R_b} - g_{m1} V_{gs1}$$

$$= -\frac{V_{out}}{R_b} - g_{m1} \left(V_{in} + \frac{R_s}{R_b} V_{out} \right)$$

In ex. $V_{out} = r_{o1} I_{o1} + V_{s1}$


$$V_{out} = r_{o1} \left(-\frac{V_{out}}{R_b} - g_{m1} \left(V_{in} + \frac{R_s}{R_b} V_{out} \right) \right) - \frac{R_s}{R_b} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m1} r_{o1} R_b}{R_b + R_s + r_{o1} + g_{m1} r_{o1} R_s}$$

si $\lambda = 0$


$$\frac{V_{out}}{V_{in}} = \frac{r_{o1} (-g_{m1} R_b)}{r_{o1} \left(1 + \frac{R_b}{r_{o1}} + \frac{R_s}{r_{o1}} + g_{m1} R_s \right)} \\ = \frac{-g_{m1} R_b}{1 + g_{m1} R_s}$$

2

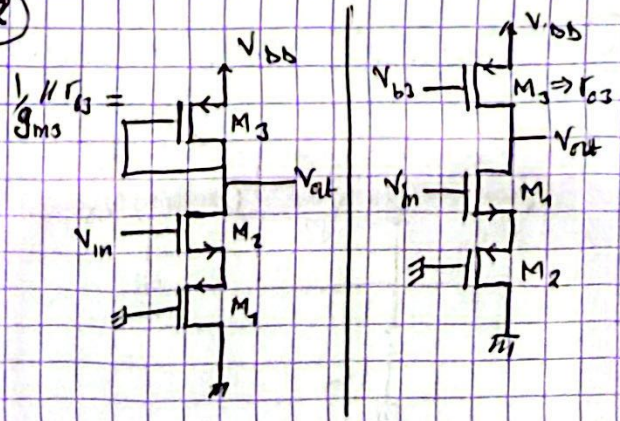

EXERCISE 3

1

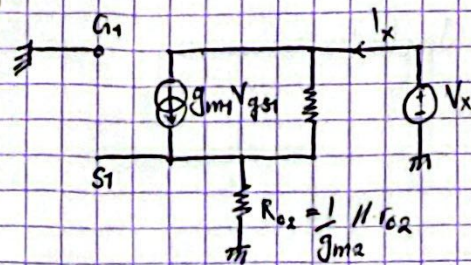

$$\text{with } R_{out} = \frac{V_x}{I_x}$$

$$V_{gs1} = V_{g1} - V_{s1} = -V_{s1} = -R_{o2} I_x$$

$$* \text{ Current } I_{o1} = I_x - g_{m1} V_{gs1} = I_x + g_{m1} R_{o2} I_x$$

$$* V_x = r_{o1} I_{o1} + R_{o2} I_x \\ = (r_{o1} (1 + g_{m1} R_{o2}) + R_{o2}) I_x$$

$$R_{out} = \frac{V_x}{I_x} = r_{o1} + R_{o2} + g_{m1} r_{o1} R_{o2}$$


$$\text{with } R_{o2} = \frac{1}{g_{m2}} \parallel r_{o2} = \frac{r_{o2} \cdot \frac{1}{g_{m2}}}{r_{o2} + \frac{1}{g_{m2}}} = \frac{r_{o2}}{1 + g_{m2} r_{o2}}$$

$$R_{out} = r_{o1} + \frac{1}{g_{m2}} \parallel r_{o2} + g_{m1} r_{o1} \left(\frac{1}{g_{m2}} \parallel r_{o2} \right)$$

* si $\lambda = 0$

$$R_{out} = r_{o1} + \frac{1}{g_{m2}} + \frac{g_{m1} r_{o1}}{g_{m2}}$$

②

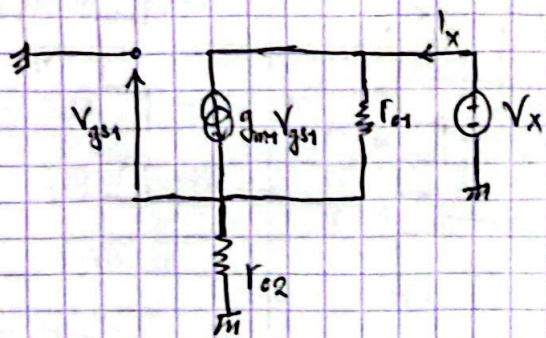

with analog in question (1)

$$R_{out} = r_{o1} + r_{o2} + g_m r_{o1} r_{o2}$$

$$R_{out} \approx g_m r_{o1} r_{o2}$$